

Total No. of Questions : 8]

SEAT No. :

PC2820

[6352]-44

[Total No. of Pages : 2

S.E. (Computer Engineering)

DIGITAL ELECTRONICS AND LOGIC DESIGN

(2019 Pattern) (Semester - III) (210245)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Attempt Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8.
- 2) Neat diagram must be drawn wherever necessary.
- 3) Assume suitable data, if necessary.

- Q1)** a) Design sequence generator using counter for sequence 1001001. [6]
b) Difference between sequential and combinational circuit. [6]
c) Explain the working of Ring counter. [6]

OR

- Q2)** a) What is MOD counter? Design MOD-6 counter using 7490. [6]
b) Design 2 bit synchronous up counter using MS-JK flip flop. Draw the circuit diagram. [6]
c) Explain in details the working of 3 bit bidirectional shift register. [6]

- Q3)** a) Draw the block diagram of PLA device and explain. [6]
b) Draw an ASM chart for 2 bit Up counter using mode control line [6]
When M = 1 : Up counting and
When M = 0 : remains in same state

- c) A combinational Circuit is defined by the following function : [5]
 $F1(A,B,C) = \sum m(0,1,2,4)$
 $F2(A,B,C) = \sum m(1,3,5,6)$
Implement this circuit with PLA.

OR

- Q4)** a) Design PLA for following function : [6]
 $F1 = A'B'C' + A'B'C + A'BC + ABC$
 $F2 = A'B'C + A'BC' + AB'C + ABC'$
b) What is an ASM chart? Name the elements of an ASM chart and define each of them. [6]
c) Implement 4 : 1 multiplexer using suitable PAL. [5]

P.T.O.

- Q5)** a) Compare TTL and CMOS families and also draw CMOS-open drain output. [6]
- b) Draw 2 i/p standard TTL NAND gate with Totem pole. Explain operation of transistor. (ON/OFF) with suitable input conditions and truth table. [6]
- c) Explain the Tristate logic and Tristate TTL inverter. [6]

OR

- Q6)** a) Explain TTL open collector. [6]
- b) Define the following terms and mention the standard values for TTL logic Family: [6]
- i) Noise Margin
 - ii) Fan Out
 - iii) Power Dissipation
- c) Draw and explain the circuit diagram of CMOS Inverter. [6]

- Q7)** a) Explain the Memory organization of the microprocessor. [6]
- b) Draw and explain 4-bit Multiplier circuit using ALU and shift registers. [6]
- c) Explain the basic arithmetic operations can be performed by using IC 74181. [5]

OR

- Q8)** a) What is Microprocessor? Explain the system bus in brief. [6]
- b) Draw and explain the block diagram of Microprocessor with its Functional units. [6]
- c) What are various functional units of microprocessors? Explain ALU in brief. [5]

x

x

x