

Total No. of Questions : 4]

SEAT No. :

PE-543

[Total No. of Pages : 2

[6578]-16

S.E. (Electronics & Computer Engineering) (Insem.)

ELECTRONIC CIRCUITS

(2019 Pattern) (Semester - III) (204202)


Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates :

- 1) Answer Q.1 or Q.2, & Q.3 or Q.4
- 2) Figures to the right side indicates full mark.
- 3) Draw neat diagram wherever necessary.
- 4) Assume suitable data, if necessary.

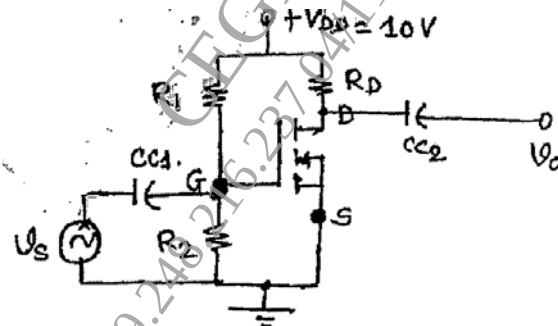- Q1) a) Explain drain & transfer characteristics of N- EMOSFET. [5]
- b) Explain any two non-ideal current voltage characteristics of MOSFET transistor. [5]
- c) For the circuit diagram shown in figure 1, calculate V_{DS} , I_D & V_{GS} . [5]




Assume : $R_1 = 10 \text{ M}\Omega$, $R_2 = 3.6 \text{ M}\Omega$, $K_n = 0.5 \text{ mA/V}^2$, $V_{TN} = 1.5 \text{ V}$

OR

- Q2) a) Draw common source of E-MOSFET amplifier and explain its modes of operation. [5]
- b) Draw the ac equivalent circuit of a CS MOSFET amplifier and draw its small signal equivalent. [5]

P.T.O.

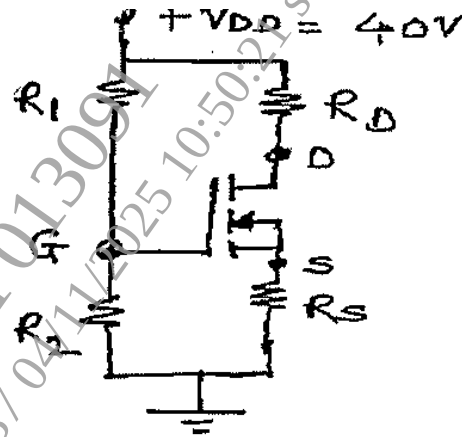
- c) For the circuit shown in figure 2. Calculate I_{DQ} , V_{DSQ} and V_D . Assume : $R_1 = 22 \text{ M}\Omega$, $R_D = 3 \text{ k}\Omega$, $R_2 = 18 \text{ M}\Omega$, $V_{TN} = 3 \text{ V}$, $R_S = 0.82 \text{ k}\Omega$ $K_n = 0.12 \text{ mA/V}^2$, $V_{GS} = 10.48 \text{ V}$ [5]



- Q3) a) Mention the effect of negative feedback on amplifier's performance such as 1. Gain 2. i/p and o/p impedance 3. Sensitivity 4. Band width. 5. Stability. [5]
 b) Draw circuit diagram of wein bridge oscillator and explain its working. [5]
 c) Explain MOSFET as Diode/Resistor [5]

OR

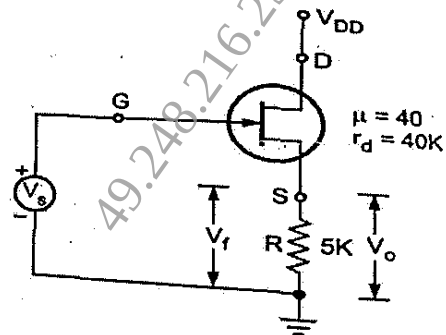- Q4) a) Identify topology of feedback and determine A_{vf} , R_{if} , R_{of} for the amplifier shown in figure. For the MOSFET $\mu = 40$, $r_d = 40 \text{ K}$. [5]



- b) Draw circuit diagram of Phase shift Oscillator and explain its working. [5]
 c) Compare different types of feedback topologies with respect to different parameter. [5]

