

[6578]-14

S.E. (Electronics/E & TC Engineering) (Insem.)

ELECTRICAL CIRCUITS

(2019 Pattern) (Semester - III) (204183)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4.
- 2) Figures to the right indicate full marks.
- 3) Neat diagrams and wave forms must be drawn wherever necessary.
- 4) Assume suitable data if necessary.
- 5) Use of nonprogrammable calculator is allowed.

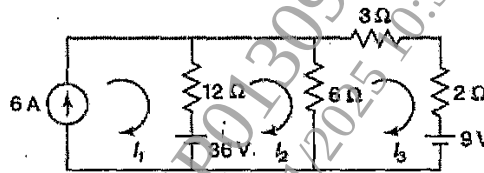
Q1) a) Find the current through the $2\ \Omega$ resistor in the network of Fig. 1 [5]

Fig.1

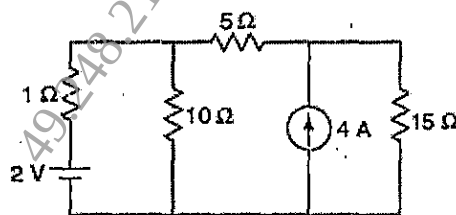
b) Using Norton's theorem, find the current through the $10\ \Omega$ resistor in the network shown in Fig.2. [5]

Fig.2

c) Find the power delivered by the 50 V source in the network Fig.3.[5]

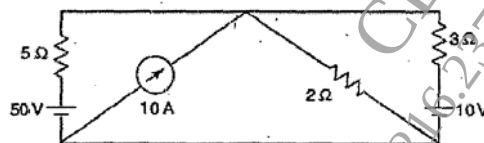


Fig.3

P.T.O.

OR

- Q2) a)** Using super node analysis, determine the current in the $5\ \Omega$ resistor for the network shown in Fig.4. [5]

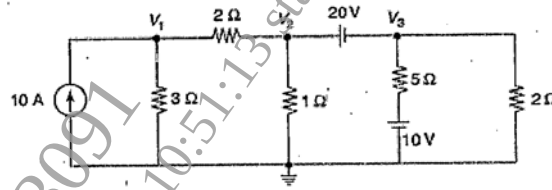


Fig.4

- b)** Using Thevenin's theorem, find the current through the $1\ \Omega$ resistor in Fig.5. [5]

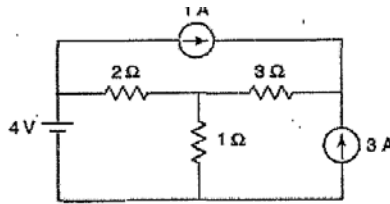


Fig.5

- c)** State Kirchhoff's voltage and current laws. [5]

- Q3) a)** A series R-L circuit is driven by DC Voltage source V . A voltage source is connected in series circuit through a switch K which is closed at $t=0$. Find expression for current through inductor for $t > 0$. Sketch the variation of $i(t)$ against time. [7]

- b)** In the given network of fig.6, the switch is closed at $t = 0$. With zero current in the inductor, find i , di/dt and di^2/dt^2 at $t = 0^+$. [8]

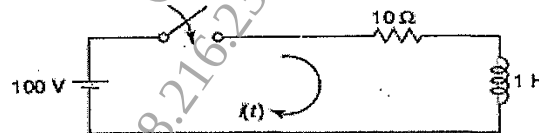


fig.6

OR

- Q4) a)** Derive the equation for the complementary solution for Voltage across capacitor for driven R-C Circuit. Draw natural Response of the Circuit for various values of t . [7]

- b)** In the network of Fig.7 the switch is closed at $t = 0$. With the capacitor uncharged, find value for i , di/dt and di^2/dt^2 at $t = 0^+$. [8]

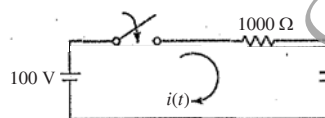


fig.7

